

Name:	Program:	Lab ID :
Exp No:	Section	Date:

### Carey Foster's Bridge (CFB)

-----

Determine the specific resistance of the given wire material.

### MARKS DISTRIBUTION

	Max. Marks	Marks Obtained
Pre - lab preparation	10	
Observation	15	
Calculation	15	
Result	05	
Viva	05	
Total	50	

Staff signature with date



## CAREY FOSTER'S BRIDGE

**Aim:** To determine (i) The specific resistance of the material of a wire and (ii) the unknown resistance of the given wire.

**Apparatus Required:** Meter bridge, Leclanché cell, two equal resistances, variable resistance box, unknown resistance, wire, high resistance, switches, galvanometer, jockey.

**Formula:**

(i) Resistance of the given coil of wire  $X = R + (l_1 - l_2) \rho \quad \Omega \quad (1)$

(ii) Specific resistance of the given coil of wire  $S = \frac{X\pi r^2}{L} \quad \Omega\text{m} \quad (2)$

Symbol	Description	Unit
X	Unknown resistance	$\Omega$
R	Known value of resistance in the resistance box	$\Omega$
$l_1, l_2, l_3$ and $l_4$	Balancing lengths	m
$\rho$	Resistivity of the bridge wire	$\Omega/\text{m}$
r	Radius of the given coil of wire	m
L	Length of the given wire	m

### PART I - Determination of $\rho$ (Resistance per unit length)

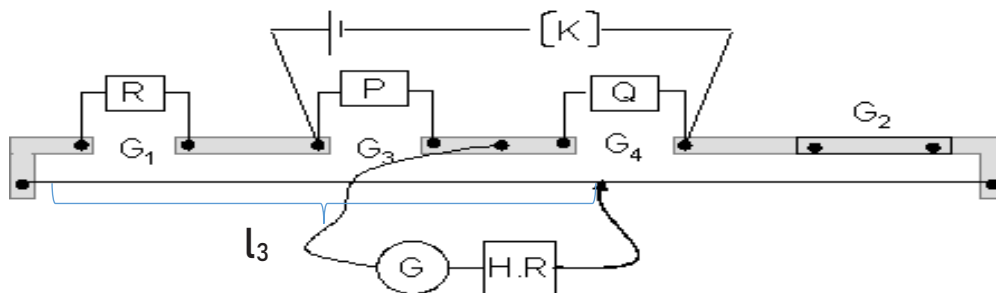


Fig 1- R in the left gap and the right gap shorted

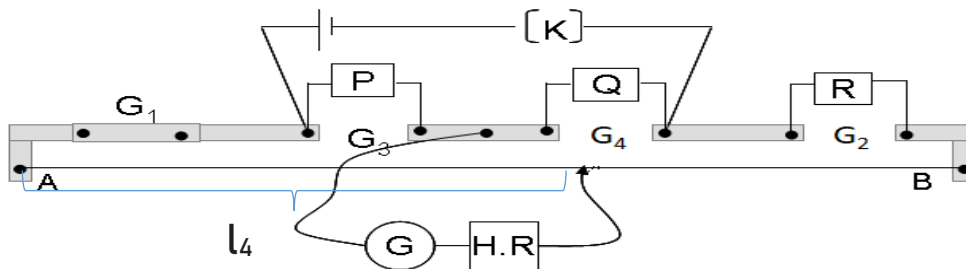


Fig 2 – R in the right gap and the left gap shorted

### PART II -Determination of unknown resistance

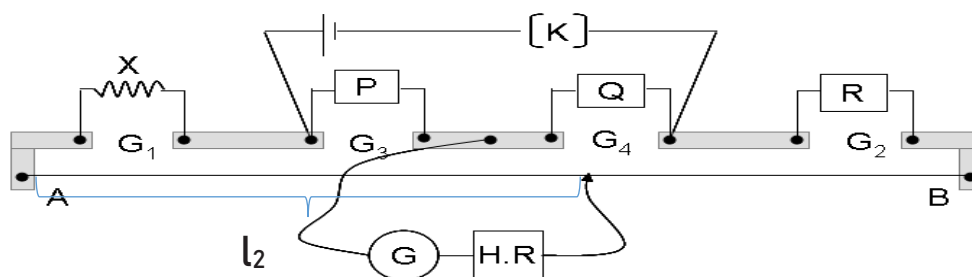


Fig 3 – Unknown resistance X in the left gap

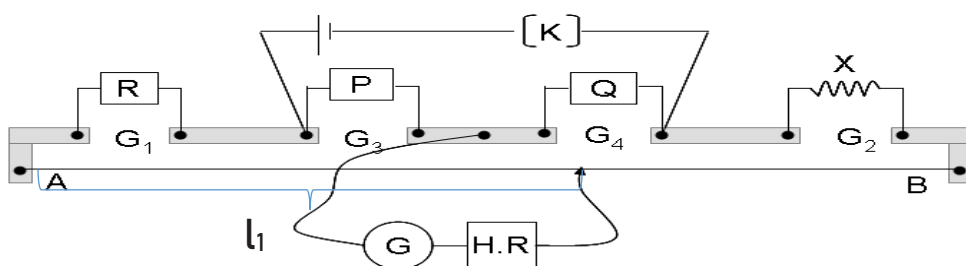


Fig 4 - Unknown resistance X in the right gap

**Principle:**

Let two equal resistances P and Q be connected in gaps  $G_3$  and  $G_4$ . Let a known resistance R be connected in gap  $G_1$  and unknown resistance X in gap  $G_2$ . Let  $l_1$  be the balance length measured from the end A (with known resistance R in the left gap). Therefore balancing length corresponding to X is  $(100 - l_1)$

$$\text{Therefore } \frac{P}{Q} = \frac{R + l_1\rho + \alpha}{X + (100 - l_1)\rho + \beta} \quad (3)$$

Where  $\rho$  = resistance per unit length of the bridge wire and  $\alpha$  and  $\beta$  are the end corrections at the ends A and B. If the experiment is repeated with R and X interchanged in the gaps, and if  $l_2$  is the balancing length measured from the same end A,

$$\frac{P}{Q} = \frac{X + l_2\rho + \alpha}{R + (100 - l_2)\rho + \beta} \quad (4)$$

From the two equations, we get,

$$X = R + (l_1 - l_2)\rho$$

Instead of resistance X, let a thick copper strip be connected in the gap  $G_2$ . i.e,  $X = 0$ .

Let  $l_3$  be the balancing length measured from the end A (with known resistance R in gap  $G_1$ )

With R in gap  $G_2$  and the copper strip connected in  $G_1$ , let  $l_4$  be the balancing length measured from the same end A.

Using the above equation,

$$0 = R + (l_3 - l_4)\rho$$

$$\text{Or, } \rho = \frac{R}{l_3 - l_4}$$

Specific resistance,  $S = \frac{\pi r^2 X}{L}$ , where r is the radius and L, the length of the wire.

**Procedure:**

**Part I To determine the resistance/unit length ( $\rho$ ) of the bridge wire.**

- Connections are made as shown in the Figure 1. P and Q are two equal resistances.
- A low range resistance box R is connected in gap  $G_1$  and short circuit to gap  $G_2$  using a thick copper strip of Zero resistance.
- A small resistance (order of  $0.1\Omega$ ) is introduced in R. The balancing length  $l_3$  from the end A is noted.

d) The resistance R and the copper strip are interchanged in the gaps. (Refer Fig 2).

The balancing length  $l_4$  from the end A is again determined.

e) Hence  $\rho = \frac{R}{l_3 \sim l_4}$  is calculated. The experiment is repeated for different values of R.

f) The mean value of  $\rho$  is calculated.

## Part II To determine the unknown resistance (X):

a) Instead of copper strip, the coil of unknown resistance of length l is connected in gap  $G_1$  (refer Fig 3)

b) The balancing lengths  $l_1$  and  $l_2$  are determined with R in the right and left extreme gaps respectively.

c) Knowing  $\rho$ , the value X is calculated using  $X = R + (l_1 - l_2)\rho$ .

d) The experiment is repeated for different values of R and the mean value of X is taken.

e) Measuring the radius r using screw gauge and using the given length l of the coil, the specific resistance is calculated.

## Observations:

### (i) Determination of $\rho$

Resistance, R ( $\Omega$ )	Balancing Length with R in		$(l_3 \sim l_4)$ (m)	$\rho = \frac{R}{(l_3 \sim l_4)} \Omega/m$
	Left gap ( $l_3$ ) (m)	Right gap ( $l_4$ ) (m)		

Mean  $\rho = \underline{\hspace{2cm}} \Omega / m$

**(ii) Determination of X**

Resistance, R ( $\Omega$ )	Balancing Length with R in		$(l_1 - l_2)(m)$	$X = R + (l_1 - l_2)\rho$ ( $\Omega$ )
	Left gap ( $l_1$ ) (m)	Right gap ( $l_2$ ) (m)		

(iii) Radius of the wire (r) = \_\_\_\_\_  $\times 10^{-3}$  m      Mean X = \_\_\_\_\_  $\Omega$

(iv) Length of the wire (L) = \_\_\_\_\_ m

$$\text{Specific resistance } S = \frac{\pi r^2 X}{L} = \quad = \quad \Omega \text{ m}$$

**Result:**

(i) The unknown resistance of the given coil of wire (X) = \_\_\_\_\_  $\Omega$

(ii) Specific resistance of the material (S) = \_\_\_\_\_  $\Omega \text{ m}$

**Signature of Faculty In-charge**

**Sample viva questions:**

1. What is the principle of Carey-Foster's bridge?
2. What is specific resistance?
3. When is Carey-Foster's Bridge more sensitive?

## WORKSHEET